

Apodization of coupled cavity array for waveguide quantum electrodynamics: design and simulation

– Hybrid Quantum Circuit Laboratory (HQC) –

Travaux pratiques IV, Physics Master EPFL

submitted by

Daniele Cucurachi

January, 2022

Daniele Cucurachi
`daniele.cucurachi@epfl.ch`
Student ID: 328929

Supervisors

1st: Dr. Vincent Jouanny
2nd: Prof. Pasquale Scarlino

École polytechnique fédérale de Lausanne (EPFL)

Contents

| | | |
|----------|--|-----------|
| 1 | Introduction and Motivations | 1 |
| 2 | Materials and Methods | 1 |
| 2.1 | Apodization in arrays of lumped-element resonators | 2 |
| 2.2 | Softwares and tools | 4 |
| 2.3 | Workflow | 4 |
| 2.3.1 | Optimal capacitance values determination | 4 |
| 2.3.2 | LTspice/Cadence simulations and design code | 5 |
| 2.3.3 | Design optimization with $Z_0 = 50 \, \Omega$ | 6 |
| 2.3.4 | Design optimization with $Z_0 = 500 \, \Omega$ | 11 |
| 3 | Results and Conclusions | 12 |
| 3.1 | Results | 12 |
| 3.2 | Conclusions | 13 |
| A | Appendix | 16 |

1 Introduction and Motivations

In the present work we aim to optimize the design of a coupled resonator waveguide QED to obtain flat transmission on a defined frequency range through apodization. In order to reach apodization we slightly modify the physical parameters of the resonators at both ends of the waveguide device so that the reflections cancel out the Fabry–Perot resonances at the resonant frequencies. This leads to a broadening of the characteristic peaks usually observed in transmission for coupled cavity arrays. Under optimal conditions, investigated by Chak et al. [1], we can exploit these broadenings to obtain flat transmission on a frequency band whose width depends on the number of resonators in the waveguide and on their coupling strength.

Apodized coupled resonator waveguides have been used for filtering applications as they operate as band-pass filters [2]. However, in recent years these devices have captivated more interest because of their possible use in slow light applications [3]. Slow light devices are based on the idea that the dispersion relation in periodic structures flattens at the transmission band edges. Since the group velocity is defined by the derivative of the dispersion relation, it is therefore small in regions where the dispersion relation goes flat, meaning that around the transmission band edges we can achieve both large transmission and low group velocity. These devices can be used to study non-Markovian dynamics i.e. dynamics of physical systems with memory of the past interactions [4].

Superconducting coplanar waveguide resonators have been also used to achieve strong coupling regime, paving the way for a multitude of new investigations [5, 6]. In addition, they represent an ideal platform to study quantum dynamics of systems interacting with a continuum of EM modes (multimode coupling).

2 Materials and Methods

In the following section I am going to provide a detailed account of the procedure that was followed in completing the project and the tools that were adopted. After a concise review of the theoretical background (subsection 2.1) I will present the softwares used for simulations (subsection 2.2) and the workflow (subsection 2.3) that guided the entire project, reporting all the relevant remarks and observations.

Note that in Appendix A is reported the python code used for the resonator waveguide design.

In the following section I am going to provide a detailed account of the procedure that was followed in completing the project and the tools that were adopted. After a concise review of the theoretical background (subsection 2.1) I will present the softwares used for simulations (subsection 2.2) and the workflow (subsection 2.3) that guided the entire project, reporting all the relevant remarks and observations.

Note that in Appendix A is reported the python code used for the resonator waveguide design.

2.1 Apodization in arrays of lumped-element resonators

We consider an array of $n = 8$ resonators, all featuring the same parameters, except for the first two and the last two.

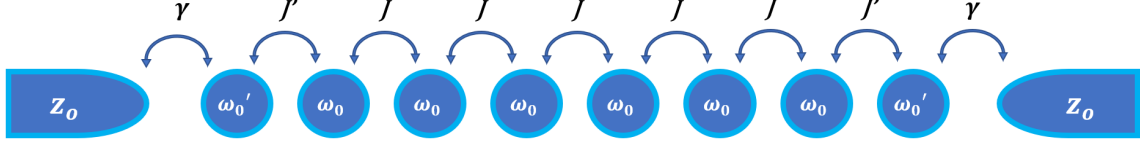


Figure 1: *Coupled resonators waveguide schematic. ω_0 and ω'_0 are the resonators resonant frequencies while J and J' are the coupling strengths. γ is the energy decay rate of the edge sites*

We describe the resonators array using the tight-binding formalism, assuming periodic boundary conditions and considering only nearest-neighbor coupling. The corresponding n -site Hamiltonian is the following:

$$H = \begin{pmatrix} \omega'_0 + i\gamma & J' & 0 & & & & & \\ J' & \omega_0 & J & & & & & \\ 0 & J & \omega_0 & & & & & \\ & & & \dots & & & & \\ & & & & \omega_0 & J & 0 & \\ & & & & J & \omega_0 & J' & \\ & & & & 0 & J' & \omega'_0 + i\gamma & \end{pmatrix}$$

Where ω'_0 is the first (and last) resonator resonant frequency, J is the inter-site coupling, J' is the inter-site coupling between the first two (and the last two) resonators, γ is the energy decay rate of the edge sites due to the coupling to the measurement setup.

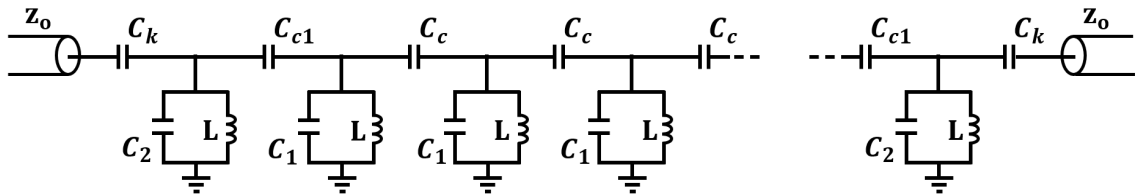


Figure 2: *Equivalent circuit representing the resonators waveguide on lumped element description. Note that we consider only nearest-neighbor coupling, secondary coupling has been neglected.*

We realize this Hamiltonian with a lumped-element resonator array coupled to transmission lines (Z_0 feedline input impedance).

The lumped-element resonator array parameters are related to the Hamiltonian parameters by:

$$J = \frac{C_c \omega_0}{2C_\Sigma} : \text{Inter-site coupling with total capacitance } C_\Sigma = C + 2C_c \text{ and resonant frequency } \omega_0 = \frac{1}{\sqrt{LC_\Sigma}}$$

$$J' = \frac{C_{c1} \omega'_0}{2C_{\Sigma'}} : \text{First two (and last two) resonators coupling with total capacitance } C_{\Sigma'} = C_k + 2C_2 + C_{c1} \text{ and resonant frequency } \omega'_0 = \frac{1}{\sqrt{LC_{\Sigma'}}}$$

$$\gamma = \frac{C_k^2 Z_0 \omega_0}{C_\Sigma^2 Z_r} : \text{Energy decay rate of the edge sites, with } Z_r = \sqrt{L/C_\Sigma}$$

In order to reach optimal apodization and obtain a flat passband in transmission, the conditions proposed by Chak and coworkers are the following [1]:

$$\begin{aligned} \omega'_0 &= \omega_0 \\ J' &= \sqrt{2}J \\ \gamma/2 &= 2J \sin(\psi) \end{aligned}$$

where $\psi = \pi/2$ (best matching at the middle of the band) or $\psi = \pi/4$ (best matching at the band edges). Considering the limit $C > C_k \gg C_{c1}, C_c$, we can meet these conditions with the following capacitances values:

$$\begin{aligned} C_{c1} &= \sqrt{2}C_c \\ C_k &= \sqrt{\frac{2C_c \sin(\psi)}{Z_0 \omega_0}} \\ C_1 &= C - (C_{c1} - C_c) \\ C_2 &= C - (C_{c1} + C_k - 2C_c) \end{aligned}$$

Where the first two conditions optimize the capacitances values to have the best result, while the last two ensure that $\omega'_0 = \omega_0$.

In [section 3](#) LTspice simulations have been used to prove that the values derived through these equations give indeed the best result: even with a small number of resonator, flat transmission is observed on a well defined frequency range proportional to the number of resonators.

2.2 Softwares and tools

In the current subsection I am going to briefly present the softwares used for simulations and the python library used to design the resonators waveguide.

LTspice and Cadence Microwave Office: circuit design softwares. High performance SPICE simulation software, schematic capture and waveform viewer with enhancements and models for easing the simulation of analog circuits.

Sonnet Software: EDA software solutions. Note that, despite Sonnet and LTspice have been both used to calculate the transmission spectrum, LTspice simulations are based on a circuit diagram that models the device while Sonnet simulates by numerically calculating Maxwell equations point by point on a 2-D representation of the real design. for high-frequency RF/MW electromagnetic analysis.

ANSYS: 3D electromagnetic (EM) simulation software for designing and simulating high-frequency electronic devices.

gdspsy library: Python module that allows the creation of GDSII stream files for micro and nano fabrication.

2.3 Workflow

The following subsection is dedicated to the presentation of the project workflow: I will provide an overview of the resonators waveguide design process, starting from the equations and finishing with the final waveguide design that will be fabricated.

2.3.1 Optimal capacitance values determination

The first step consisted in exploiting the equations, derived in [subsection 2.1](#), in order to find the best capacitance values for the resonator waveguide to obtain a flat band in transmission. Since we have more parameters than equations: 6 parameters to determine

$$C, C_c, C_{c1}, C_k, C_1, C_2$$

and only 4 equations,

$$C_{c1} = \sqrt{2}C_c$$

$$C_k = \sqrt{\frac{2C_c \sin(\psi)}{Z_0 w_0}}$$

$$C_1 = C - (C_{c1} - C_c)$$

$$C_2 = C - (C_{c1} + C_k - 2C_c)$$

we are free to assign arbitrary values to two of these parameters and successively derive the others. This comes really in handy when considering that, in circuit quantum electrodynamics, we have a narrow range of possible values for these capacitances due to the physical limits of the devices. We can therefore exploit these degrees of freedom to choose some convenient values, easy to realize.

Note that, in the present analysis, we are not considering L_0 and Z_0 since these parameters are fixed. Z_0 is the input feedline impedance for which we have only two possible values: 50Ω , and 500Ω which can be reached by tapering. On the other hand, we take L_0 as a fixed parameter ($L_0 = 38.8nH$) because we want a large inductance since it is needed for metamaterial waveguides [7, 8, 9], paving the way for future applications of the devices designed in this work. When increasing L_0 we induce a redshift in the resonators resonant frequency (defined as $w_0 = \frac{1}{\sqrt{LC_\Sigma}}$), therefore we cannot use inductance values larger than $\approx 40 nH$, otherwise the resonant peaks in transmission would appear in a range of the frequency spectrum we are not able to probe with the available lab instruments.

I started with $Z_0 = 50\Omega$ and I chose as starting point the following values:

$$C_c = 0.43 fF \quad , \quad C = 25 fF$$

where C_c represents the coupling capacitance between two neighbouring resonators in the waveguide and C is the coupling capacitance between a single resonator and ground, since these values have been already obtained for other devices in the past, therefore we knew they were achievable in practise.

Using Chak's equations we successively derived the values for the other parameters:

| C_c | C | C_k | C_{c1} | C_1 | C_2 |
|---------|-------|----------|----------|----------|---------|
| 0.43 fF | 25 fF | 19.63 fF | 0.61 fF | 24.82 fF | 5.62 fF |

Table 1: Values derived through Chak's equations starting from $C_c = 0.43 fF$, $C = 25 fF$

2.3.2 LTspice/Cadence simulations and design code

Once a proper choice of the starting parameters has been made, I simulated the transmission spectrum of the resonator waveguide using LTspice and Cadence Microwave Office. Simulations and parametric analysis have been used to confirm that the derived parameter values were indeed the ones giving the best results. As it is shown in [Figure 4](#), the closer the parameters are to the derived ones, the flatter is the band we observe in transmission.

After the simulations confirmed this starting set of values, I designed the first prototype of the device. In order to optimize and speed up the designed process I coded a program in Python, using the gdspy library, that prints out a fully customizable gds file of the resonators waveguide (the Python code is reported in [Appendix A](#))

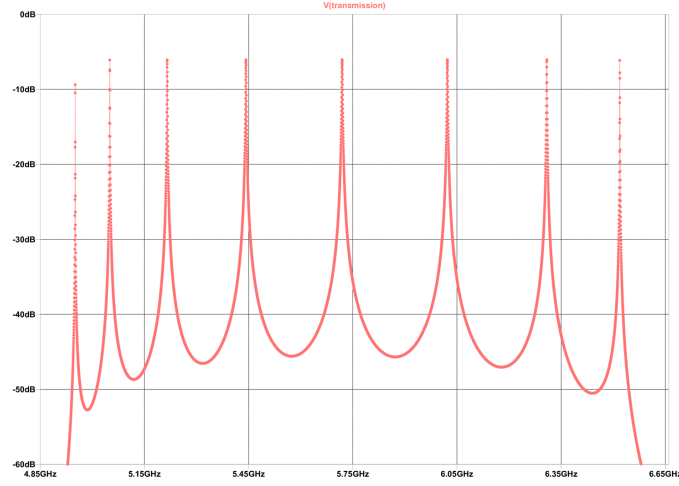


Figure 3: *Transmission vs frequency for a standard coupled resonators waveguide not apodized (the parameters are set as: $C_c = C_{c1} = C_k$ and $C_1 = C_2 = C$).*

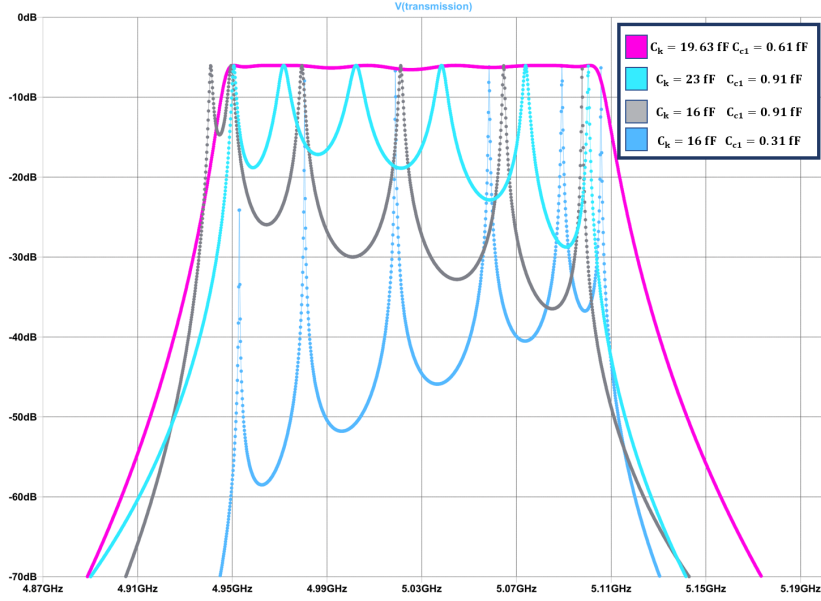


Figure 4: *Transmission spectrum for the apodized coupled resonators waveguide. The 4 traces in different colours represent 4 different set of values for the parameters C_k and C_{c1} . It is clear that the best result is achieved when using the values derived from Chak's equations: for $C_k = 19.63$ fF and $C_{c1} = 0.61$ fF a flat band is observed in transmission.*

2.3.3 Design optimization with $Z_0 = 50 \Omega$

The gds file has been then used to run a simulation on ANSYS in order to numerically calculate the capacitance matrix of this first design. The capacitance matrix provides, for each element of the waveguide (single resonators, ground, feedline capacitors), the coupling capacitances with respect to the other elements. The capacitance matrix

values, results of the simulation, have been then compared to the desired capacitance values derived from the equations. This first comparison allowed me to understand how far the starting design was from the optimal one I was looking for.

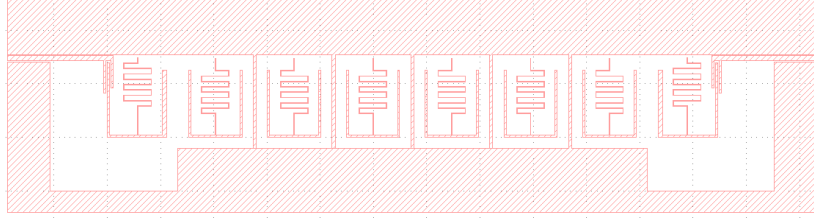


Figure 5: *First waveguide design: the ground piece between the first (last) and second (last second) resonators has been removed in order to reduce the capacitance to ground for the first resonator (C_2). Note that, for ANSYS simulations, the resonators must be separated from the ground (as you can see in this picture) so that they can be simulated as individual elements.*

| | C_c | C | C_k | C_{c1} | C_1 | C_2 |
|-------------------------|------------------|-----------------|------------------|------------------|-----------------|-------------------|
| Desired cap values | 0.43 fF | 25 fF | 19.63 fF | 0.61 fF | 24.82 fF | 5.62 fF |
| First design cap values | ≈ 1.5 fF | ≈ 17 fF | ≈ 5.5 fF | ≈ 2.5 fF | ≈ 15 fF | ≈ 14.5 fF |

Table 2: *Comparison between ANSYS simulation results and optimal capacitance values derived from Chak's equation*

The next phase has been characterized by a trial and error approach aimed to understand how different modifications in the physical structure of the device affected the capacitances values. To this purpose I have run several simulations on ANSYS changing each time a different parameter in the waveguide: for example capacitors thickness, capacitors length, distances between resonators and ground, and so on.

This analysis showed that, as expected, we can modify the coupling capacitance between two elements in the waveguide by:

- Increasing or decreasing the distance between the two elements. However, we cannot have a too large separation since we would have problems with the lithography process (used to fabricate the waveguide): first of all it would imply longer time and higher costs for the process, and it would also increase the probability of errors in the making.
- Modifying the thickness of the two elements. However, we cannot decrease it too much or an element which is supposed to be a capacitor will start behaving as an inductor in practise.
- Modifying the exposed surface between the two elements (see example in [Figure 6](#)).

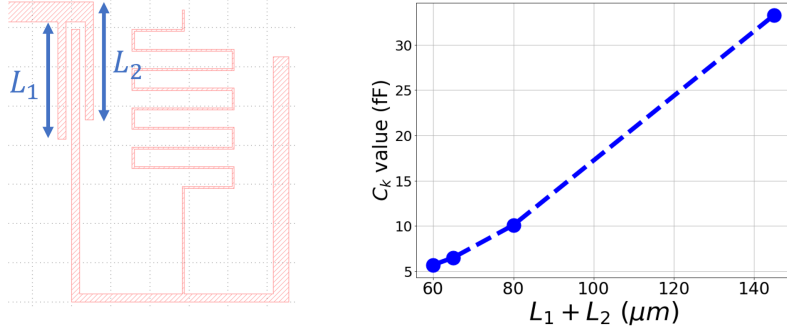


Figure 6: Impact of the feedline capacitor length on C_k value. C_k represents the coupling capacitance between the first resonator and the feedline capacitor. Note that there are other waveguide features that strongly affect the value of C_k : the distance between the feedline capacitor and the resonator capacitor, the thickness of the capacitors.

After this initial study, I started modifying the waveguide design in order to achieve the optimal capacitance values. This step by step process gradually converged towards the optimal waveguide design: at each step the design was modified and simulated with ANSYS, then the simulations results, compared with the desired capacitance values, provided a feedback which suggested how to further modify the design.

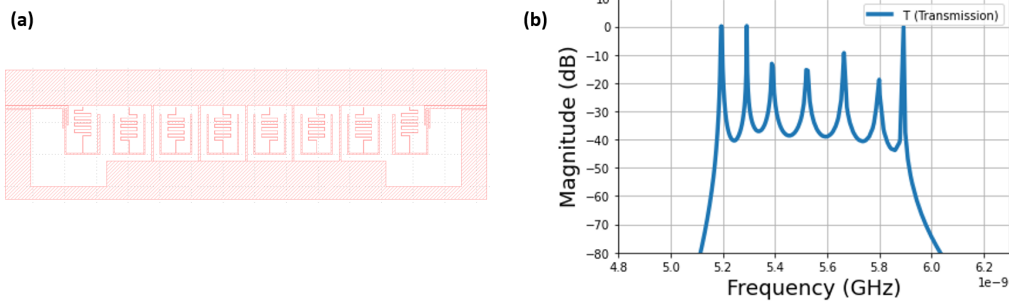


Figure 7: Sonnet simulation of the first waveguide design. The transmission spectrum shows several well defined peaks meaning that the waveguide is not apodized.

As shown Figure 5, the ground between the first and second resonators has been removed in order to decrease the capacitance to ground for the first resonator with respect to the others (indeed for the optimal capacitance values we have $C_2 \ll C$) and increase the capacitive coupling between the first two resonators (since $C_{c1} > C_c$).

During this design optimization process, together with ANSYS simulations, Sonnet simulations (Figure 7) were used to monitor the evolution of the transmission spectrum.

Thanks to this process I managed to design a waveguide that met the optimal parameters for C, C_c, C_{c1}, C_k, C_1 . However, the simulations showed that, for this kind of device, obtaining $C_2 = 5.62$ fF was not feasible (where C_2 is the coupling capacitance between the first/last resonators and ground). Even pushing the design to the limits the C_2 value calculated by ANSYS did not get smaller than $\approx 10 - 11$ fF (Figure 8).

I could not even lower the values of C_c and C_{c1} (where $C_{c1} = \sqrt{2}C_c$) to increase the optimal value of C_2 (where $C_2 = C - (C_{c1} + C_k - 2C_c)$) because they both have a very narrow range of achievable values ($\approx 0.1 - 3$ fF) and they were already quite small. If C_c and C_{c1} are too small, the waveguide does not work properly since these two values are proportional to the capacitive coupling between the resonators $J \propto C_c$ and $J' \propto C_{c1}$.

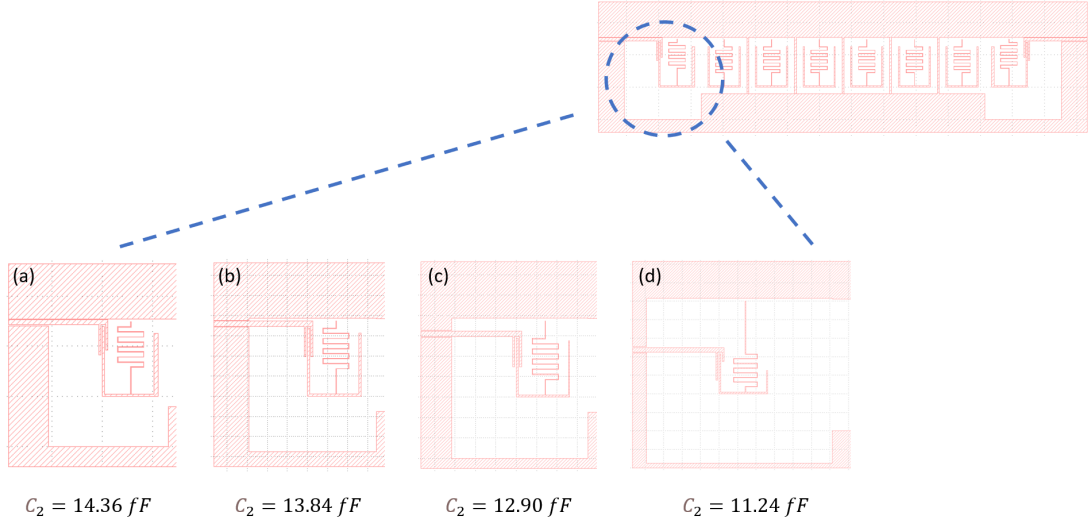


Figure 8: Attempts to decrease C_2 (first and last resonators capacitance to ground) in order to achieve the optimal value. In design (a) and (b) the separation between the first resonator and the ground is increased, in (c) and (d) the separation is increased and the first resonator capacitor thickness is reduced.

None of the proposed designs reach the optimal value for C_2 and it is not possible to increase further the distance from the ground since this would give problems during fabrication with the lithography process.

In order to overcome this problem, the solution was finding a new optimal capacitance values set. Therefore I exploited again the equations presented in [subsection 2.1](#), imposing $C_2 = 13$ fF this time. Note that C_2 has to be kept as small as possible because it is directly related to C value: following Chak's equations, the larger is C_2 the larger C is gonna be. Already for $C_2 \approx 15-20$ fF, C reaches values which are not achievable in practise for this kind of devices. Imposing $C_2 = 13$ fF allows to have achievable values for both C_2 and C .

Starting from $C_2 = 13$ fF and $C_c = 1$ fF, which ensures a good coupling between the resonators, I derived the new set of optimal capacitance values reported in [Table 3](#).

| C_c | C | C_k | C_{c1} | C_1 | C_2 |
|---------|----------|----------|----------|----------|----------|
| 1.00 fF | 48.00 fF | 35.29 fF | 1.41 fF | 47.58 fF | 13.30 fF |

Table 3: New set of optimal values derived starting from $C_2 = 13$ fF and $C_c = 1$ fF.

This new set contains all achievable capacitance values. However, in this case we have the resonators resonant frequencies:

$$f_0 = \frac{1}{\sqrt{LC_\Sigma}2\pi} \approx 3.6 \text{ GHz}$$

This is a problem for us because we cannot probe this range of frequencies with the instruments available in our lab.

 


Figure 9: ANSYS Capacitance matrix of the optimal design for the case $Z_0 = 50 \Omega$

The only remaining parameter that can be tuned is L_0 , even though reducing L_0 means giving up on high inductance to ground for our device. We have that:

$$L = L_\square \frac{l}{w}$$

Where L_\square is the inductance per square, l and w are the length and the width of the inductor wire. By shortening the inductor wire by almost half of its original length, I reduced L_0 from 38.8 nH to 20 nH, taking the resonators resonant frequencies to ≈ 5 GHz.

With this new set of parameters, adopting the same optimization procedure described before, I obtained the design shown in Figure 9. Note that the thickness of the resonators capacitors have been increased and the distance between the resonators and ground has been strongly decreased in order to achieve large C values. On the other hand, reaching a large C_k has been easy since the interdigitated feed line capacitor allows a good control over this parameter.

Note also that, despite the capacitance values calculated through ANSYS simulation (shown in Figure 9) are not close to the optimal values (shown in Table 3), this design is the one giving the best results for the case $Z_0 = 50 \Omega$.

2.3.4 Design optimization with $Z_0 = 500 \Omega$

We can achieve an input impedance of $Z_0 = 500 \Omega$ by tapering. This second case turned out to be much easier with respect to the first one since a larger value of Z_0 allows to reach apodization with lower capacitance values with respect to the previous case, easier to achieve, keeping at the same time a large L_0 ($L_0 = 38.8 \text{ nH}$).

Following the same process used for the $Z_0 = 50 \Omega$ case, I derived the set of optimal values reported in [Table 4](#).

| C_c | C | C_k | C_{c1} | C_1 | C_2 |
|---------|----------|---------|----------|----------|----------|
| 1.00 fF | 22.70 fF | 9.35 fF | 1.41 fF | 22.20 fF | 13.98 fF |

Table 4: New set of optimal values for the case $Z_0 = 500 \Omega$

 


Figure 10: ANSYS Capacitance matrix of the optimal design for the case $Z_0 = 500 \Omega$

Again, by a step by step design optimization, we obtained the design reported in [Figure 10](#) for this new case.

3 Results and Conclusions

In the following section will be presented the results and the conclusions of my work: I will show the two final designs, products of the optimization process presented in [subsection 2.3](#), and the relative transmission spectra.

3.1 Results

The optimal design for the case $Z_0 = 50 \Omega$ is reported in [Figure 11](#):

 


Figure 11: *Optimal design (a) and transmission spectrum (b) for the case $Z_0 = 50 \Omega$*

For the second case, $Z_0 = 500 \Omega$, the results are shown in [Figure 12](#):

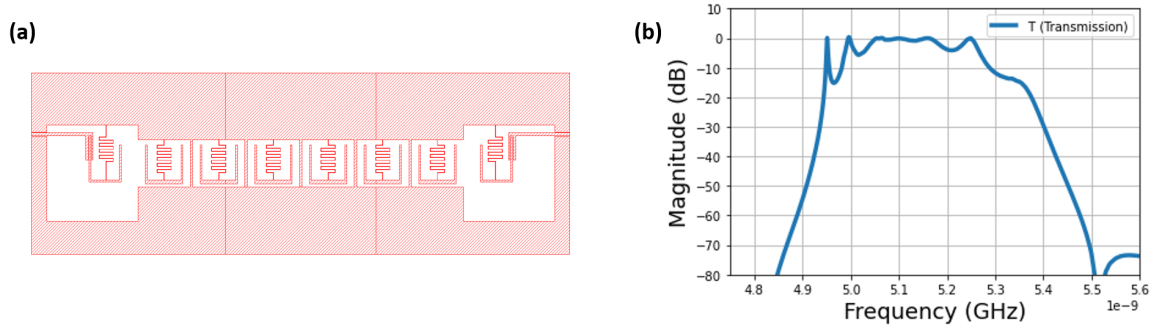


Figure 12: *Optimal design (a) and transmission spectrum (b) for the case $Z_0 = 500 \Omega$*

In [Figure 11](#) and [Figure 12](#) we can observe that both the transmission spectra feature an asymmetric shape, a shoulder is visible on the right side of the bands. This asymmetry is inherited from the resonator waveguide transmission spectrum, which already shows this characteristic when not apodized (see [Figure 3](#)).

Another common characteristic is the presence of two residual peaks on the left side of the bands. We observe that these peaks are less pronounced in the second case ($Z_0 = 500 \Omega$), where we also have a larger frequency range with flat transmission: ≈ 0.3 GHz, compared to ≈ 0.15 GHz for the $Z_0 = 50 \Omega$ case. In order to mitigate these oscillations at the band edges we could use a larger number of resonators: with

more resonators we can increase the extent of the band and have flat transmission on larger frequency range.

In [Figure 13](#) are pictured the two different resonators designs for the two waveguides. In the first case ($Z_0 = 50 \Omega$) the capacitor has a wider and thicker bottom part in order to reach a larger value for the capacitance to ground $C = 48$ fF, while $C = 22.7$ fF in the case $Z_0 = 500 \Omega$. On the other hand, in order to compensate this larger capacitance value, the inductor wire is reduced by half in this case so that the resonators resonant frequencies (defined as $f_0 = \frac{1}{2\pi\sqrt{LC_\Sigma}}$, where C is the dominant factor in $C_\Sigma = C + 2C_c$) falls into the range 4.5 GHz - 6 GHz.

 


Figure 13: *Comparison between the two different resonators designs for the two waveguides*

3.2 Conclusions

Starting from the equations derived in [subsection 2.1](#), we successfully designed two coupled resonators waveguides, with different input impedances $Z_0 = 50 \Omega$ $Z_0 = 500 \Omega$, optimized to achieve apodization. Both devices clearly show flat transmission respectively in the frequency ranges 5.6 – 5.8 GHz ($Z_0 = 50 \Omega$ case) and 5 – 5.3 GHz ($Z_0 = 500 \Omega$ case), according to Sonnet simulations. These frequency ranges are optimal to study waveguide-SC qubits multimode coupling since superconducting qubits usually have frequencies in the range 4 – 8 GHz [\[10, 11, 12\]](#).

The waveguide designs have been derived through the process explained in [subsection 2.3](#). In order to optimize and speed up the design process we developed a Python program that prints out a fully customizable gds file of the resonators waveguide (see [Appendix A](#)).

References

- [1] Philip Chak and J. E. Sipe. “Minimizing finite-size effects in artificial resonance tunneling structures”. In: *Opt. Lett.* 31.17 (Sept. 2006), pp. 2568–2570. DOI: [10.1364/OL.31.002568](https://doi.org/10.1364/OL.31.002568). URL: <http://www.osapublishing.org/ol/abstract.cfm?URI=ol-31-17-2568>.
- [2] J. Capmany et al. “Apodized coupled resonator waveguides”. In: *Optics express* 15 (Sept. 2007), pp. 10196–206. DOI: [10.1364/OE.15.010196](https://doi.org/10.1364/OE.15.010196).
- [3] Simone Gasparinetti Simon Mathis Jean-Claude Besse. “Microwave Waveguides with Engineered Dispersion based on Arrays of Lumped-Element Resonators”. In: *ETH Zurich, semester project* (Oct. 2017).
- [4] Vinicius S. Ferreira et al. “Collapse and Revival of an Artificial Atom Coupled to a Structured Photonic Reservoir”. In: *Phys. Rev. X* 11 (4 Dec. 2021), p. 041043. DOI: [10.1103/PhysRevX.11.041043](https://doi.org/10.1103/PhysRevX.11.041043). URL: <https://link.aps.org/doi/10.1103/PhysRevX.11.041043>.
- [5] Abdufarrukh A. Abdumalikov et al. “Vacuum Rabi splitting due to strong coupling of a flux qubit and a coplanar-waveguide resonator”. In: *Phys. Rev. B* 78 (18 Nov. 2008), p. 180502. DOI: [10.1103/PhysRevB.78.180502](https://doi.org/10.1103/PhysRevB.78.180502). URL: <https://link.aps.org/doi/10.1103/PhysRevB.78.180502>.
- [6] Andreas Wallraff et al. “Strong coupling of a single photon to a superconducting qubit using circuit quantum electrodynamics”. In: *Nature* 431 (Oct. 2004), pp. 162–7. DOI: [10.1038/nature02851](https://doi.org/10.1038/nature02851).
- [7] D. J. Egger and F. K. Wilhelm. “Multimode Circuit Quantum Electrodynamics with Hybrid Metamaterial Transmission Lines”. In: *Phys. Rev. Lett.* 111 (16 Oct. 2013), p. 163601. DOI: [10.1103/PhysRevLett.111.163601](https://doi.org/10.1103/PhysRevLett.111.163601). URL: <https://link.aps.org/doi/10.1103/PhysRevLett.111.163601>.
- [8] C. Caloz and T. Itoh. “Transmission line approach of left-handed (LH) materials and microstrip implementation of an artificial LH transmission line”. In: *IEEE Transactions on Antennas and Propagation* 52.5 (2004), pp. 1159–1166. DOI: [10.1109/TAP.2004.827249](https://doi.org/10.1109/TAP.2004.827249).
- [9] H. Wang et al. “Mode Structure in Superconducting Metamaterial Transmission-Line Resonators”. In: *Phys. Rev. Applied* 11 (5 May 2019), p. 054062. DOI: [10.1103/PhysRevApplied.11.054062](https://doi.org/10.1103/PhysRevApplied.11.054062). URL: <https://link.aps.org/doi/10.1103/PhysRevApplied.11.054062>.
- [10] Xiu Gu et al. “Microwave photonics with superconducting quantum circuits”. In: *Physics Reports* 718-719 (July 2017), pp. 1–102. DOI: [10.1016/j.physrep.2017.10.002](https://doi.org/10.1016/j.physrep.2017.10.002).
- [11] Morten Kjaergaard et al. “Superconducting Qubits: Current State of Play”. In: *Annual Review of Condensed Matter Physics* 11.1 (Mar. 2020), pp. 369–395. ISSN: 1947-5462. DOI: [10.1146/annurev-conmatphys-031119-050605](https://doi.org/10.1146/annurev-conmatphys-031119-050605). URL: <http://dx.doi.org/10.1146/annurev-conmatphys-031119-050605>.

- [12] P. Krantz et al. “A quantum engineer’s guide to superconducting qubits”. In: *Applied Physics Reviews* 6.2 (June 2019), p. 021318. ISSN: 1931-9401. DOI: [10.1063/1.5089550](https://doi.org/10.1063/1.5089550). URL: <http://dx.doi.org/10.1063/1.5089550>.

A Appendix

Python design code

```
1  # -*- coding: utf-8 -*-
2  """
3  @author: Daniele Cucurachi
4
5  FULLY CUSTOMIZABLE COUPLED RESONATORS WAVEGUIDE GDS DESIGN
6
7  the function is divided into 4 parts, each part is related to the
8  ↪ design of a specific component. In the end, all the
9  components are put together to crate the full WG. We have in order:
10
11     1) standard resonators pairs: the resonators pairs that form the
12     ↪ waveguide
13
14     2) first resonator (+ feedline capacitor): first resonator in the
15     ↪ waveguide and input feedline capacitor
16
17     3) last resonator: mirrored copy of the first resonator
18
19     4) ground design
20
21     NOTE: the various parts of the function create the negatives of the
22     ↪ components designs we need. At the end, the boolean "not" function
23     ↪ is used to subtract these negatives from a rectangle (which is the
24     ↪ ground) and we obtain the full WG
25
26  """
27
28  ### # -----
29
30  # IMPORT LIBRARIES
31
32  import numpy as np
33  import gdspy
34
35  ### # -----
36
37  def RES_WG_APO():
```

```

38
39 # define all the parameters
40
41 # NOTE: the default dimensions are micrometers (um)
42
43
44 """1) STANDARD RESONATORS PAIRS"""
45
46 # STD INDUCTOR
47
48 L = 279 # total length of the inductor wire
49 s = 4.5 # interspacing between the inductor windings
50 wid = 0.5 # width of inductor wire
51
52 compact = False # chose if compact inductor design or not
53
54 # STD CAPACITOR
55
56 A = 62 # horizontal dimension of U-capacitor
57 t = 3 # thickness of U-capacitor
58 add_t = 3 # added thickness for the bottom capacitor segment
59
60 # RESONATOR GROUND DISTANCES
61
62 dist_ground = 5 # distance between the capacitor and the ground
63 res_dist_l = 29 # left lateral distance between two resonators in
    ↳ the resonators chain
64 res_dist_r = 29 # right lateral distance between two resonators in
    ↳ the resonators chain
65 inter_cell_dist = 4 # space between the two cells containing the
    ↳ resonators
66 ind_to_ground = 10 # last inductor segment that connects the
    ↳ inductor to ground (inter_res_dist)
67 centre=(0,0) # centre where I start to draw the design
68
69
70 """2) FIRST RESONATOR + FEEDLINE CAPACITOR"""
71
72 # F INDUCTOR
73
74 Li = 279 # total length of the inductor wire
75 si = 4.5 # interspacing of turns of the inductor wire
76 wi = 0.5 # width of inductor wire
77 d_second =20 # last segment of the inductor (connection to ground.
    ↳ It defines the distance from ground at the top of the resonator
    ↳ cell)
78

```

```

79 compact_ind = False # chose if compact inductor design or not
80 separated_elements = False # chose if you want to separate the
    ↪ inductor from the GND (for ANSYS simulations)
81 separation_length = 2 # separation length for separated elements
    ↪ option
82
83 # FEEDLINE INTERDIGITATED CAPACITOR
84
85 w2 = 2 # external feedline capacitor width
86 sc = 1.5 # lateral separation between the first resonator capacitor
    ↪ and the feedline capacitor
87 y = 2 # vertical separation between the first resonator capacitor
    ↪ and the feedline capacitor
88 w = 5 # feedline width
89 w1 = 4 # width of the internal capacitor arm
90 L2 = 45 # length of the internal capacitor arm
91 L1 = 40 # length of the external capacitor arm
92 Bwg = 200 # feedline length
93
94 # F CAPACITOR
95
96 Ac = 50 # horizontal dimension of U-capacitor (without additions,
    ↪ the final effective width is = A+Ws-t+Wl)
97 tc = 3 # thickness of U-capacitor (note that the thickness of the
    ↪ capacitor wide arm can be tuned individually)
98 Wl = t # wide arm thickness
99 Lw = 60 # wide arm length
100 Ws = (sc + w2) # thin arm shift
101
102 # GROUND DISTANCES
103
104 dist_ground_first = 65 # distance between capacitor and ground
105 first_dist_lateral_l = 65 # left lateral distance between the
    ↪ capacitor and ground
106 first_dist_lateral_r = 28 # right lateral distance between the
    ↪ capacitor and ground
107 WG_width = 7 # feedline capacitor width
108
109 # define two parameters that will be used when creating the ground
    ↪ geometry
110
111 Lateral_l = Bwg + w1 + sc
112 Lateral_r = Ws + Ac + Wl - tc + first_dist_lateral_r
113
114
115
116 """3) LAST RESONATOR"""

```

```

117
118
119
120 """4) GROUND DESIGN"""
121
122 Height = 250 # distance between the first cell and the edge of the
123 ↪ ground piece
124 N_pairs = 3 # number of cells pairs in the waveguide (NOT including
125 ↪ the first and last cells)
126
127 """ANSYS/SONNET SIMULATION ADDED CAPACITOR THICKNESS """
128
129 # the parameter T1 offer the possibility to increase the thickness
130 ↪ of the second and last second capacitors
131 # the parameter T2 offer the possibility to increase the thickness
132 ↪ of the ground piece below the second and last second capacitors
133
134 # T1 and T2 are used to tune the capacitance to ground of the second
135 ↪ and last second capacitors indipendently from the resonators in
136 ↪ the waveguide
137
138 T1 = 0# thickness of the added capacitor piece
139
140 T2 = 0# thicnkess of the added ground piece
141
142 # -----
143 # RESONATORS WAVEGUIDE DESIGN: PART 1) 2) 3) 4)
144
145
146
147 """1) STANDARD RESONATORS PAIRS"""
148
149
150
151 # CHECK FOR DIMENSIONS MISMATCH IN THE DISTANCES BETWEEN THE
152 ↪ RESONATORS (STD RESONATORS CHAIN)
153
154 while (res_dist_l <= inter_cell_dist):

```

```

154     print("MISMATCH: res_dist_l (lateral distance between two
        ↳ resonators in the chain) is equal or smaller than
        ↳ inter_cell_dist (width of the ground in between two
        ↳ resonators cells)")
155     new = input("Enter new value for res_dist_l:")
156     res_dist_l = float(new)
157
158
159     while (res_dist_r <= inter_cell_dist):
160         print("MISMATCH: res_dist_r (lateral distance between two
            ↳ resonators in the chain) is equal or smaller than
            ↳ inter_cell_dist (width of the ground in between two
            ↳ resonators)")
161         new = input("Enter new value for res_dist_r:")
162         res_dist_r = float(new)
163
164     dist_lateral_l = (res_dist_l - inter_cell_dist)/2
165     dist_lateral_r = (res_dist_r - inter_cell_dist)/2
166
167
168
169     # PARAMETERS CALCULATIONS
170
171     # horizontal dimension of the resonators pairs (these parameters
        ↳ will be used later to draw the waveguide geometry)
172
173     Horizonta = 2*A + 2*dist_lateral_l + 2*dist_lateral_r +
        ↳ inter_cell_dist
174
175     half_res = A/2 + dist_lateral_l
176
177     #calculate horizontal dimension of inductor
178
179     b = 3/5*A - 2*t
180
181     #calculate number of windings in the inductor
182
183     if compact == False:
184         N = int((L-(ind_to_ground + (s+wid)))/(b+s))
185     else:
186         N = round((L-(ind_to_ground + (s+wid)))/(b+s))
187     # print('N: ',N)
188
189     #adapt first segment of the inductor
190
191     d_prime = (L - (N*(s+b)+ind_to_ground)) + wid
192

```

```

193     #calculate vertical dimension of capacitor
194
195     B = N*(s+wid) + d_prime + t
196
197     # define Ushape, set of points that will define the capacitor
198     ↪ geometry
199
200     U=[]
201     x0, y0 = centre[0],centre[1]
202     U.append([x0, y0])
203
204     x1, y1 = x0, y0 - B + t/2
205     U.append([x1, y1])
206
207     x2, y2 = x1 + A - t, y1
208     U.append([x2, y2])
209
210     x3, y3 = x2, y2 + B - t/2
211     U.append([x3, y3])
212
213     U = np.asarray(U)
214     centring = (A-t)/2, -B
215     U = U - centring
216
217     # additional thickness for the bottom segment of the capacitor
218
219     bottom_cap = gdspy.Rectangle((-A/2,-add_t),(+A/2,0))
220
221     #set of points that will define the meander (inductor) starting from
222     ↪ centre of U
223
224     M = []
225     v0,w0 = centre[0], centre[1]+t
226     M.append([v0,w0])
227
228     v1,ww1 = v0, w0 + d_prime - wid/2
229     M.append([v1,ww1])
230
231     for i in range(N):
232         if i%2 == 0:
233             v2, ww2 = M[-1][0] - b/2 + wid/2, M[-1][1]
234             M.append([v2,ww2])
235             v3, w3 = v2, ww2 + (s+wid)
236             M.append([v3,w3])
237             v4, w4 = v3 + (b/2 - wid/2), w3
238             M.append([v4,w4])
239             # print(i)
240         if (i+1)%2==0:

```

```

238     v5,w5 = M[-1][0] + b/2 - wid/2, M[-1][1]
239     M.append([v5,w5])
240     v6, w6 = v5, w5 + (s+wid)
241     M.append([v6,w6])
242     v7,w7 = v6 - b/2 + wid/2, w6
243     M.append([v7,w7])
244     # print(i)
245     if (i+1)==N:
246         # print('end turns:', M[-1])
247         v8,w8 = M[-1][0], M[-1][1]
248         v9, w9 = v8, w8 + ind_to_ground - wid/2
249
250         # separate the inductor from the capacitor (OPTIONAL)
251
252         if separated_elements==True:
253             w9 = w9 - separation_length
254
255         M.append([v9,w9])
256
257
258
259     # GENERATE CAPACITOR AND INDUCTOR GEOMETRIES
260
261     Upath = gdspy.FlexPath(U,t)    # capacitor
262     Mpath = gdspy.FlexPath(M,wid)  # inductor
263
264     # create the negative that will be used later to create the final
265     ↪ resonator waveguide
266
267     rec = gdspy.Rectangle(-(A/2) + dist_lateral_l, -add_t
268     ↪ -dist_ground), ((A/2) + dist_lateral_r, B + ind_to_ground -
269     ↪ wid))
270
271     upneg = gdspy.boolean(rec, Upath, "not")
272     upneg = gdspy.boolean(upneg, Mpath, "not")
273     upneg = gdspy.boolean(upneg, bottom_cap, "not")
274
275     # create the negative of a pair of resonators spaced by
276     ↪ inter_cell_dist
277
278     upneg_mirr = gdspy.copy(upneg)    # copy the geometry
279     upneg_mirr.mirror([A/2 + dist_lateral_r + inter_cell_dist/2, 0],[A/2
280     ↪ + dist_lateral_r + inter_cell_dist/2, B])    # mirror the
281     ↪ geometry

```



```

279
280 """2) FIRST RESONATOR"""
281
282
283 # CHECK IF THERE ARE DIMENSIONS MISMATCHES
284
285 while d_second < (y+w+(WG_width-w)/2):
286     print("ERROR: dimensions mismatch, d_second smaller than y+w")
287     new = input("Enter new value for d_second:")
288     d_second = float(new)
289
290
291
292 # INDUCTOR DESIGN
293
294 #calculate horizontal dimension of inductor
295 # this inductor horizontal dimension will define the distance
↪ between the capacitors's arm and the inductor
296
297 bi = (3/5)*Ac - 2*tc
298
299 #calculate number of windings in the inductor
300
301 if compact_ind == False:
302     N = int((Li-(d_second + (si+wi)))/(bi+si))
303 else:
304     N = round((Li-(d_second + (si+wi)))/(bi+si))
305
306 #adapt start & end segment of inductor
307
308 d_prime = (Li - (N*(si+bi) + d_second)) + wi
309
310 # define set of points that will be used to draw the inductor
311
312 M = []
313 v0,w0 = centre[0], centre[1]
314 M.append([v0,w0])
315 v1,ww1 = v0, w0 + d_prime - wi/2
316 M.append([v1,ww1])
317
318 # Inductor's windings
319
320 for i in range(N):
321
322     if i%2 == 0:
323         v2, ww2 = M[-1][0] + bi/2 - wi/2, M[-1][1]
324         M.append([v2,ww2])

```

```

325         v3, w3 = v2, ww2 + (si+wi)    # ww2 cause we already defined
326         ↪ a w2 variable
327         M.append([v3,w3])
328         v4, w4 = v3 - (bi/2 - wi/2), w3
329         M.append([v4,w4])
330
331     if (i+1)%2==0:
332         v5,w5 = M[-1][0] - bi/2 + wi/2, M[-1][1]
333         M.append([v5,w5])
334         v6, w6 = v5, w5 + (si+wi)
335         M.append([v6,w6])
336         v7,w7 = v6 + bi/2 - wi/2, w6
337         M.append([v7,w7])
338
339     if (i+1)==N:
340         # print('end turns:', M[-1])
341         v8,w8 = M[-1][0], M[-1][1]
342         v9, w9 = v8, w8 + d_second + wi/2
343
344         # separate the inductor from the capacitor (OPTIONAL)
345
346         if separated_elements==True:
347             w9 = w9 - separation_length
348
349         M.append([v9,w9])
350
351     # shift the inductor (shift every point) and center it with respect
352     ↪ to the capacitor (you drew the inductor centred in (0,0))
353
354     M = np.asarray(M)
355     centring = (Ac/2)+Ws, tc
356     M = M + centring
357
358     # draw the inductor
359
360     ind = gdspy.FlexPath(M,wi)    # FIRST RESONATOR INDUCTOR GEOMETRY
361
362
363     # CAPACITOR DESIGN
364
365     # Define length of the capacitor thin arm (the left one)
366
367     Lt = N*(si+wi) + d_prime + tc
368
369     # check for dimensions mismatch

```

```

370
371 while (Lw >= (Lt+d_second)):
372     print("MISMATCH: Lw is larger than Lt+d_second, it touches the
        ↳ ground")
373     new = input("Enter new value for Lw:")
374     Lw = float(new)
375
376 while ((L2-w+sc) > (y+(Lt-tc))):
377     print("ERROR: dimensions mismatch (L2 too large)")
378     new = input("Enter new value for L2:")
379     L2 = float(new)
380
381 # define the capacitor geometry
382
383 lcap = gdspy.Curve(0, 0).L(0,Lt, tc,Lt, tc,tc, Ws+Ac-tc,tc,
        ↳ Ws+Ac-tc,tc, Ws+Ac-tc,Lw, Ws+Ac+Wl-tc,Lw, Ws+Ac+Wl-tc,0, 0,0)
384 cap = gdspy.Polygon(lcap.get_points()) # FIRST RESONATOR CAPACITOR
        ↳ GEOMETRY
385
386
387
388
389 """2) FEEDLINE CAPACITOR DESIGN"""
390
391
392 # DEFINE THE FEEDLINE CAPACITOR DESIGN
393
394 # the center (0,0) is the same used for the first resonator design
        ↳ function
395
396 wlcap = gdspy.Curve(-(sc+w1+Bwg),Lt+y).L(-(sc+w1+Bwg),Lt+y+w,
        ↳ tc+sc+w2,Lt+y+w, tc+sc+w2,Lt+y+w-L2, tc+sc,Lt+y+w-L2,
        ↳ tc+sc,Lt+y, -sc,Lt+y, -sc,Lt+y-L1, -(sc+w1),Lt+y-L1,
        ↳ -(sc+w1),Lt+y, -(sc+w1+Bwg),Lt+y)
397 wcap = gdspy.Polygon(wlcap.get_points())
398
399
400 # CREATE THE NEGATIVE of the whole resonator + waveguide capacitor
        ↳ geometry B
401
402 contour_line = gdspy.Curve(-(sc+w1+first_dist_lateral_l),

```

403

```

↪ -dist_ground_first).L((Ws+Ac+Wl-tc+first_dist_lateral_r),(-dist_ground_first),
↪ (Ws+Ac+Wl-tc+first_dist_lateral_r),(Lt+d_second),
↪ -(sc+w1+first_dist_lateral_l),(Lt+d_second),
↪ -(sc+w1+first_dist_lateral_l),(Lt+d_second-(d_second-(y+w+((WG_width/2)
↪ - (w/2))))),
↪ -(sc+w1+Bwg),(Lt+d_second-(d_second-(y+w+((WG_width/2) -
↪ (w/2))))),
↪ -(sc+w1+Bwg),(Lt+d_second-(d_second-(y+w+((WG_width/2) -
↪ (w/2))))-WG_width),
↪ -(sc+w1+first_dist_lateral_l),(Lt+d_second-(d_second-(y+w+((WG_width/2)
↪ - (w/2))))-WG_width),
↪ -(sc+w1+first_dist_lateral_l),-(dist_ground_first))
contour = gdspy.Polygon(contour_line.get_points())

```

404

405

406

```

# boolean subtraction to generate the negative

```

407

408

```

cont = gdspy.boolean(contour, wcap, "not")

```

409

410

```

co = gdspy.boolean(cont, cap, "not")

```

411

412

```

first_neg = gdspy.boolean(co, ind, "not") # NEGATIVE OF THE CELL
↪ CONTAINING FIRST RESONATOR + FEEDLINE CAPACITOR

```

413

414

415

416

417

418

```

"""3) LAST RESONATOR: mirrored copy of the first one"""

```

419

420

421

```

# CREATE A MIRRORED COPY OF THE FIRST RESONATOR

```

422

423

```

first_neg_mirr = gdspy.copy(first_neg) # copy the geometry

```

424

```

first_neg_mirr.mirror([(2*Lateral_r + N_pairs*Horizonta +
↪ (N_pairs-1)*inter_cell_dist)/2, 0],[(2*Lateral_r +
↪ N_pairs*Horizonta + (N_pairs-1)*inter_cell_dist)/2, 1*1e-6]) #
↪ mirror the geometry

```

425

426

```

# NOTE: the mirrored copy is already shifted to the right at the end
↪ of the waveguide

```

427

428

429

430

431

```

"""4) GROUND DESIGN"""

```

432

```

433
434 # CREATE THE GROUND RECTANGULAR GEOMETRY
435
436 # calculate the ground rectangle length
437
438 Rec_len = 2*Lateral_l + 2*Lateral_r + N_pairs*Horizonta +
↳ (N_pairs-1)*inter_cell_dist
439
440 #create the ground rectangle
441
442 ground = gdspy.Rectangle((-Lateral_l),-(Height)), (Rec_len -
↳ Lateral_l, B + Height))
443
444
445 # SUBTRACT THE NEGATIVES
446
447 # create a cell array with the negatives of the standard resonators
↳ pairs
448
449 Res_pair_cell = gdspy.Cell("std_resonators_pair_reference")
450
451 Res_pair_cell.add(upneg)
452
453 Res_pair_cell.add(upneg_mirr)
454
455 res_array = gdspy.CellArray(ref_cell=Res_pair_cell, columns=N_pairs,
↳ rows=1, spacing = (Horizonta + inter_cell_dist, 0),
↳ origin=(Lateral_r + (half_res), 0)) # res_array type is cell
↳ array
456
457
458 # added capacitor thickness for ANSYS and Sonnet simulations
459 # check if there is a dimension mismatch
460
461 while ((T1+T2) >= dist_ground):
462     print("MISMATCH: ")
463     new = input("Enter new value for T1:")
464     T1 = float(new)
465     new = input("Enter new value for T2:")
466     T2 = float(new)
467
468
469 rec1 = gdspy.Rectangle((Lateral_r + dist_lateral_l,0),(Lateral_r +
↳ dist_lateral_l + A,-T1))
470

```

```

471 rec2 = gdspy.Rectangle((Lateral_r +
↪ dist_lateral_l, -dist_ground), (Lateral_r + dist_lateral_l + A,
↪ -dist_ground + T2)) # this has this weird geometry cause I want
↪ to maximize the distance between the the first resonator
↪ capacitor and the ground
472
473 rec3 = gdspy.Rectangle((Lateral_r + Horizontal*N_pairs +
↪ inter_cell_dist*(N_pairs-1) - (dist_lateral_l + A)
↪ , 0), (Lateral_r + Horizontal*N_pairs + inter_cell_dist*(N_pairs-1)
↪ - (dist_lateral_l + A) + A, -T1))
474
475 rec4 = gdspy.Rectangle((Lateral_r + Horizontal*N_pairs +
↪ inter_cell_dist*(N_pairs-1) - (dist_lateral_l +
↪ A), -dist_ground), (Lateral_r + Horizontal*N_pairs +
↪ inter_cell_dist*(N_pairs-1) - (dist_lateral_l + A) + A,
↪ -dist_ground + T2))
476
477
478 res_array = gdspy.boolean(res_array, rec1, "not")
479 res_array = gdspy.boolean(res_array, rec2, "not")
480 res_array = gdspy.boolean(res_array, rec3, "not")
481 res_array = gdspy.boolean(res_array, rec4, "not")
482
483
484 # add the negatives of the components to one single cell (called
↪ "negatives")
485
486 negatives = gdspy.Cell("negatives")
487
488 negatives.add(res_array)
489
490 negatives.add(first_neg)
491
492 negatives.add(first_neg_mirr)
493
494
495 # subtract the negatives
496
497 WG = gdspy.boolean(ground, negatives, "not")
498
499 main = gdspy.Cell("Full_WG")
500 main.add(WG)
501
502
503 # RETURN: cell with the complete WG
504
505 return main

```

```
506
507
508 ### -----
509
510 # PRINT A GDS FILE OF THE CHOSED DESIGN
511
512 main = RES_WG_APO()
513
514 lib = gdspy.GdsLibrary()
515
516 lib.add(main)
517
518 gdspy.LayoutViewer(lib)
519
520 # Save the library in a file called 'first.gds'
521
522 lib.write_gds('file_name.gds')
```